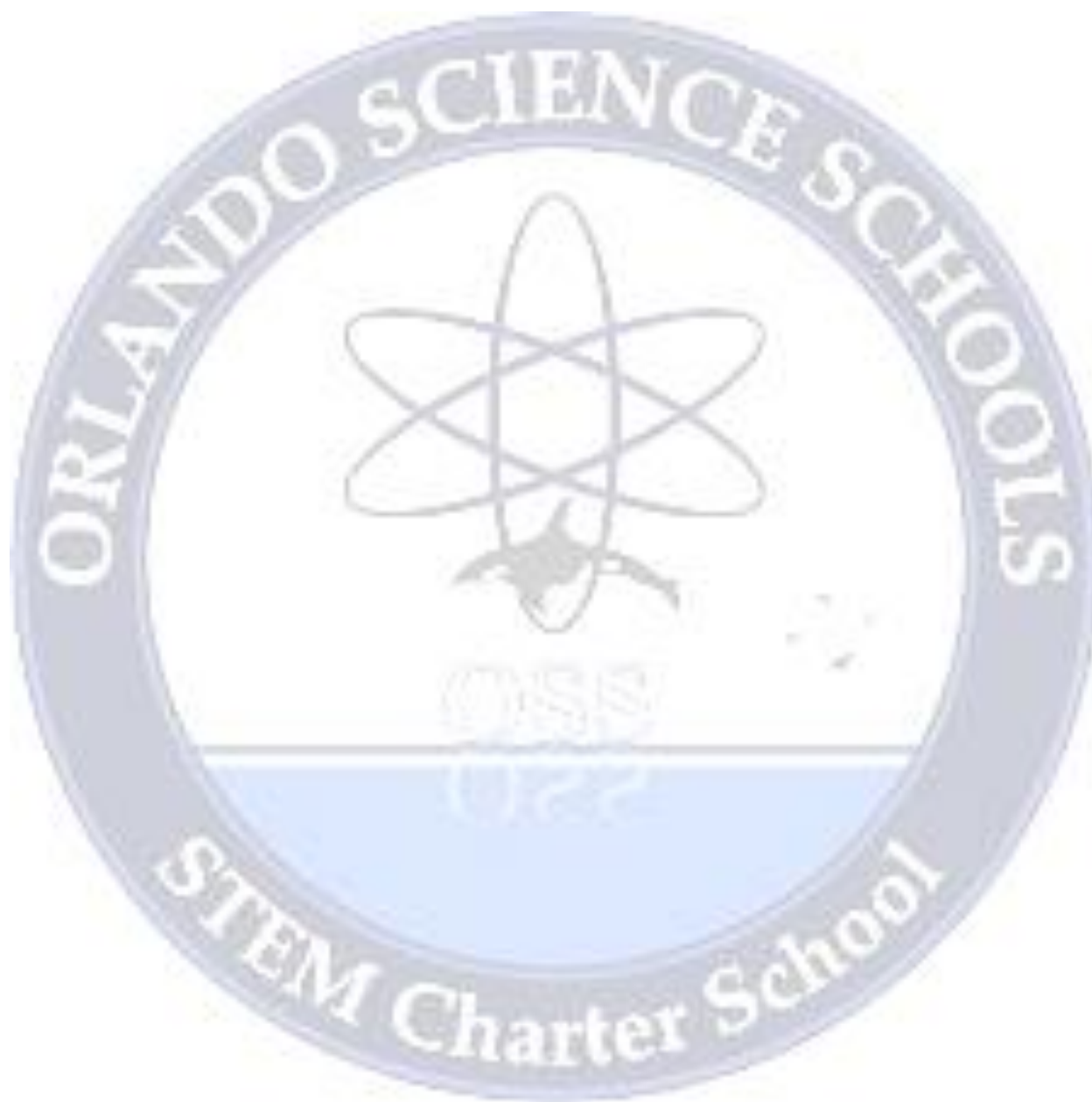


Circuit Lab
Division C ANSWER KEY

School: _____

Team Number: _____

Team Members: _____



Part I

- 1 C (2 points)
- 2 C (2 points)
- 3 A (2 points)
- 4 B (2 points)
- 5 D (2 points)
- 6 A (2 points)
- 7 B (2 points)
- 8 D (2 points)
- 9 B (2 points)
- 10 A (2 points)
- 11 Ronald Portugal (2 points)
- 12 Hans Oersted (2 points)
- 13 Donald Macadie (2 points)
- 14 Friedrich Drexler (2 points)
- 15 Thomas Edison (2 points)

Part II

$$F = k_e \frac{q_1 q_2}{r^2}$$

1 Use the formula , resulting in $8.99 * 10^9 * \frac{(24*10^{-3})(45)}{64^2} = 2.37 * 10^6$;

This is a repulsion, as they have the same sign, concluding that they repel against one another. Additionally, since the force is positive, it must be a repulsion. (6 points [3 points for correct number and 3 points for correct sign])

- 2 Coulomb's Law (2 points)

3 **Coulomb's Constant (AKA electrostatic constant)** is $8.99 * 10^9 \frac{N*m^2}{C^2}$ (2 points)

4 The law was first published in 1785 by French physicist **Charles-Augustin de Coulomb** (3 points[1 point for the correct year and 2 points for correct person])

5 Solving, you get $\frac{1}{\frac{1}{C_3+C_2+C_1} + \frac{1}{C_4+C_5}} = \frac{1}{\frac{1}{500*(10^{-3})+500*(10^{-3})+1} + \frac{1}{500*(10^{-3})+5}} = \frac{1}{\frac{1}{2} + \frac{1}{5.5}} = 1.47$ (10 points)

6 $Q = C * V \rightarrow Q = 1.47 * 20 = 29.33$ (5 points)

7 $V_c = V_o(1 - e^{-t/(RC)}) \rightarrow 10 \left(1 - e^{\frac{-23}{250}}\right) \rightarrow 0.88$ (5 points)

8 $Q = C * V \rightarrow 10V * 5F = 50$ (2 points)

Part III

1 **B** (2 points)

2 **C** (2 points)

3 **C** (2 points)

4 **True** (2 points)

5 **A** (2 points)

6 **Direct Current must be a straight line, while alternate current should be a sine wave** (4 points [2 point for correct DC line, 2 point for correct AC line])

7 **A** (2 points)

Part IV

1 $N_p \times I_p = N_s \times I_s \rightarrow 5 \times 10A = 20 \times I_s \rightarrow I_s = 2.5A$ or $5/2A$ (3 points)

2 $N_p \times V_s = N_s \times V_p \rightarrow 5 \times 400V = 20V \times N_s \rightarrow N_s = 100$ (3 points)

3:

A – Windings (2 points)

B – Brushes (2 points)

C – Rotor (2 points)

D – Commutator (2 points)

E – Magnet (2 points)

F – Stator (2 points)

G – Terminals (2 points)

4 Permanent Magnet, Series, Shunt, Compound (4 points [1 point for each correct])

5 Induction and Synchronous (2 points [1 point for each correct])

6 Rotor (2 points)

7 Stator (2 points)

Part V

1 Variable DC Power Supply (2 points)

2 Potentiometer (2 points)

3 Fuse (2 points)

4 Zener Diode (2 points)

5 Integrated Circuit (2 points)

6 Motor (2 points)

7 $\frac{12}{(6+2)} = 1.5A$ or $3/2A$ (3 points)

8 $\frac{8}{(4+2)} = 1.33A$ or $4/3A$ (3 points)

9 $\frac{4}{3}A + \frac{3}{2}A = 2.83A$ or $17/6A$ (3 points)

10 $1.5A \times 6\Omega = 9A$ (3 points)

11 $1.33A \times 4\Omega = 5.33A$ or $16/3A$ (3 points)

12 $2.83A \times 2\Omega = 5.67A$ or $17/3A$ (3 points)

13

Step 1: Solve the first big area (R1-R9):

R1-R5 $\rightarrow 120 \Omega$

R6-R9 $\rightarrow 100 \Omega$

R1-R9 $\rightarrow 600/11 \Omega$

Step 2: Solve R10-R14:

R13-R14 $\rightarrow 20 \Omega$

R11-R14 $\rightarrow 600/17 \Omega$

R10-R14 $\rightarrow 600/23 \Omega$

Step 3: Solve R1-R15:

Add up to get $22930/253 \Omega$ or 90.63Ω (20 points)

Part VI

1 Positive or + (2 points)

2 False (2 points)

3 Silicon PN Junction (2 points)

4 $v_{in} \times gain = v_{out} \rightarrow gain = -\frac{R_f}{R_{in}} \rightarrow v_{out} = -15V$ (4 points)

5 $gain = -\frac{R_f}{R_{in}} \rightarrow -\frac{3}{4}$ or -0.75 (4 points)

6 $v_{in} \times gain = v_{out} \rightarrow gain = 1 + \frac{R_2}{R_1} \rightarrow v_{out} = 35V$ (4 points)

7 $gain = 1 + \frac{R_2}{R_1} \rightarrow v_{out} = \frac{7}{4}$ or 1.75 (4 points)

Part VII

1 1 (2 points)

2 1 (2 points)

3 0 (2 points)

4 1 (2 points)

5 0 (2 points)

6 1 (2 points)

7 1 (2 points)

8 1 (2 points)

9 0 (2 points)

10 1 (2 points)

11 0 (5 points)