

SSSS - 2019

Circuit Lab **KEY**

DIVISION C

Written by: terence.tan

Sections:

1. General Knowledge and Historical Facts
2. DC Circuits
3. Capacitors
4. Magnetism & EM Induction
5. Digital Logic
6. Misc.

General Knowledge and Historical Facts

- 1) There is no potential difference in a single wire. For electrons to move there must be a difference in electric potential
- 2) Tesla
- 3) Ohm
- 4) Volta
- 5) Faraday
- 6) Hertz
- 7) $\text{kg} \cdot \text{m} \cdot \text{s}^{-2}$
- 8) $\text{s}^4 \cdot \text{A}^2 \cdot \text{m}^{-2} \cdot \text{kg}^{-1}$
- 9) $\text{m}^2 \cdot \text{kg} \cdot \text{s}^{-3} \cdot \text{A}^{-2}$
- 10) $\text{kg} \cdot \text{m}^2 \cdot \text{s}^{-2} \cdot \text{A}^{-1}$
- 11) light emitting diode
- 12) leyden jar
- 13) capacitor
- 14) Lead, Gold, Tungsten, rubber, teflon
- 15) A
- 16) B

DC Circuits

- 1) -2.85A
- 2) 3.745V

I1- Bottom left loop

I2- Bottom middle loop

I3- Bottom right loop

I4- Top Middle loop

$$(I_2 - I_1) \times R_1 + (I_2 - I_4) \times R_2 + (I_2 - I_3) \times R_4 = 0$$

$$(I_2 - 2) \times 2 + (I_2 - I_4) \times 4 + (I_2 + 4) \times 3 = 0$$

$$2I_2 - 4 + 4I_2 - 4I_4 + 3I_2 + 12 = 0$$

$$9I_2 - 4I_4 = -8 \quad (1)$$

$$I_4 \times R_3 - 4V + I_4 \times R_5 + (I_4 - I_2) \times R_2 = 0$$

$$I_4 \times 1 - 4 + I_4 \times 2 + (I_4 - I_2) \times 4 = 0$$

$$7I_4 - 4I_2 = 4 \quad (2)$$

Solving equations 1 and 2, we obtain:

$$I_2 = -4.047\text{A}, I_4 = 4.47\text{A}$$

$$1) I_x = I_2 - I_1 = -2.851\text{A}$$

$$2) I_{R2} = I_2 - I_4 = 0.9362\text{A}$$

$$V_{R2} = I_{R2} \times R_2 = 0.9362 \times 4 = 3.7447\text{V}.$$

3) 8.4V

Use Loop rule:

$$+12V - 6V - 2I - 3I = 0$$

$$6V - 5I = 0$$

$$I = 1.2A$$

$$V_{R_2} = IR_2 = (1.2A)(2\Omega) = 2.4V$$

$$\Delta V = V_2 + V_{R_2} = 6V + 2.4V = 8.4V$$

4) 1.2V

Use Loop rule:


$$+12V + 6V - 2I - 3I = 0$$

$$18V - 5I = 0$$

$$I = 3.6A$$

$$V_{R_4} = IR_4 = (3.6A)(2\Omega) = 7.2V$$
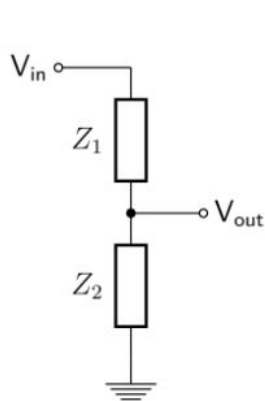
$$\Delta V = V_{R_4} - V_6 = 7.2V - 6V = 1.2V$$



$$V_{out} = V_{in} \cdot \frac{R_2}{R_1 + R_2}$$

5)

$Z_1 = R_1$ $Z_2 = R_2$; As long as the formula to the right is fulfilled. Ex) $R_1 = 9V$ $R_2 = 6V$

6) 10A

7) 27V


8) 21.6KJ

Capacitors

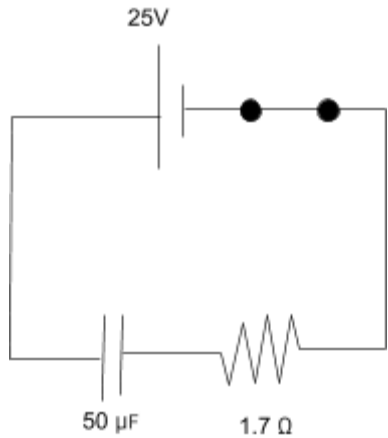1) 85 microseconds

1 time constant has passed once $V = 25V/e = 9.1969V$

$V = 9.1969V$ at $t \approx 8.5 \cdot 10^{-5}s = 85$ microseconds



2)

$$\tau = RC$$

$$(85 \times 10^{-6} \text{ s}) = (1.7 \, \Omega) C$$

$$C = 50 \, \mu\text{F}$$

3) 5 time constants

4) $5 \, \mu\text{F}$

$$2 \, \mu\text{F} / C = 10 \, \mu\text{F} / 25 \, \mu\text{F}$$

$$C = 5 \, \mu\text{F}$$

5) $3.83 \, \text{pF}$

$$5 \text{ cm}^2 = 0.0005 \text{ m}^2$$

$$C = \epsilon_0 A K / D$$

$$C = (8.85 \times 10^{-12} \text{ F} \cdot \text{m}^{-1}) (0.0005 \text{ m}^2) (2.6) / (3 \times 10^{-3} \text{ m})$$

$$C = 3.835 \text{ pF}$$

6) $15.3 \, \mu\text{C}$

Magnetism and Em Induction

1) $1672 \, \text{V}$

$$30,000 \text{ cm}^2 = 3 \text{ m}^2$$

$$\text{EMF} = AB\omega \cos(\theta)$$

$$\text{EMF} = (3 \text{ m}^2)(3.62 \text{ T})(154 \text{ rad/s}) \cos(0)$$

$$\text{EMF} = 1672.44 \text{ V}$$

2) C

3) D

4) B

5) C

6) C

7) the two wires will attract and move closer

Digital logic

1)

A	B	A'	B'	Z
0	0	1	1	1
0	1	1	0	1
1	0	0	1	1
1	1	0	0	0

2)

A	B	A'	B'	A'B	AB'	Z
0	0	1	1	0	0	0
0	1	1	0	1	0	1
1	0	0	1	0	1	1
1	1	0	0	0	0	0

3) NAND



4) XOR




5) $\Sigma=(0,1,4,5,6,7)$

6) $F(X,Y,Z)=y'+z$


7) $F(X,Y,Z)=x'+y+z'$

Misc

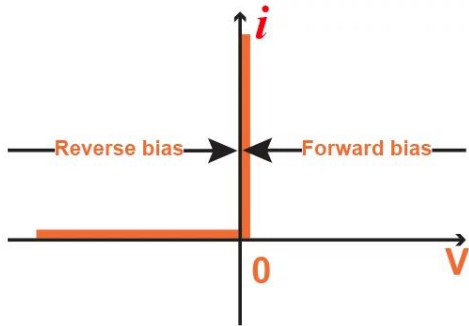

1)

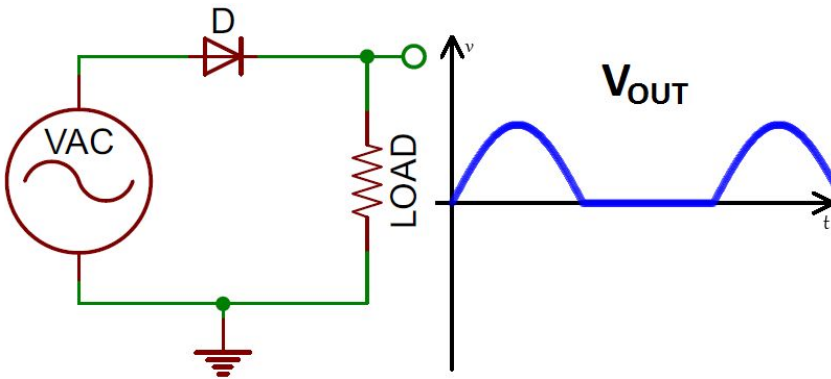2) Current that the diode will leak when a reverse voltage (not in the direction that the diode allows) is applied to it. Occurs in realistic diodes.



3)

4) AC transmission has a more efficient voltage step-up and step-down system using transformers but DC is more difficult. (full credit)

Easier to convert AC to DC than the other way around (only 1pt)

5) It switches the electromagnets from north and south and back again (spins the motor)

6) -3