
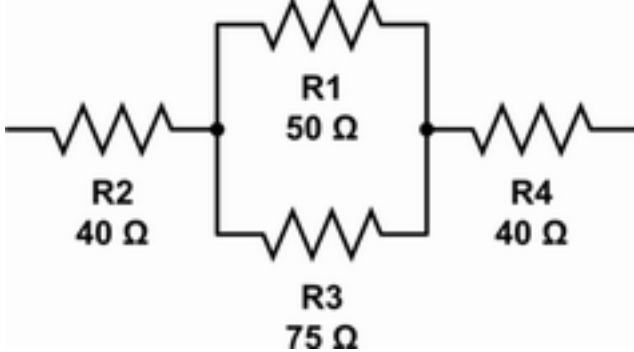


Circuit Lab

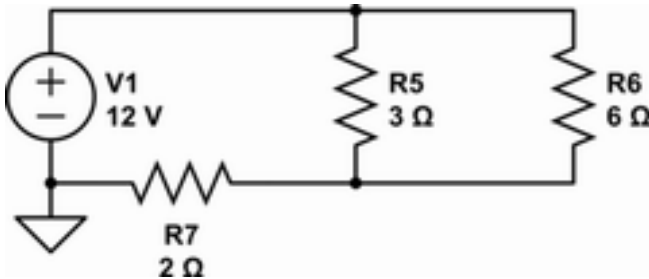1. What is the total resistance from point the left end of the circuit to the right end?



2. Find the current passing through each resistor.




R5: _____ R6: _____ R7: _____

3. What voltage is, conservatively, considered to be dangerous to humans?

- A. 10 V
- B. 30 V
- C. 60 V
- D. 120 V

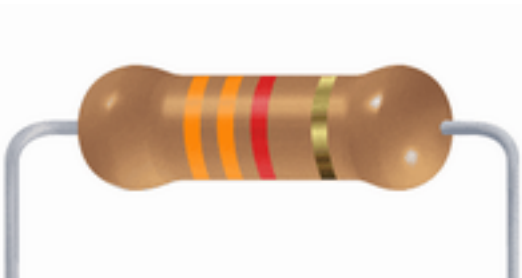4. What is the resistance of this resistor?



Colors are orange, orange, red, gold (left to right)




5. Identify this component:

Name:

Function:

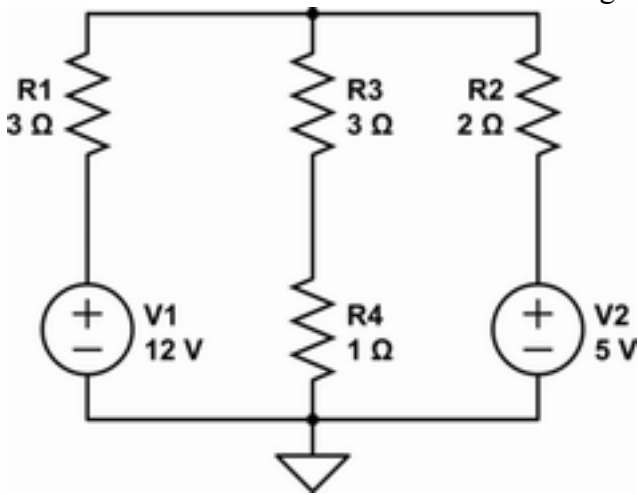6. Find the magnitude of the voltage drop across each resistor.



R1: _____ R2: _____ R3: _____

R4: _____


7. Which of the following types of batteries cannot be recharged?

- A. Lead-Acid
- B. Nickel-Zinc
- C. Alkaline
- D. Lithium-Ion


8. What is the SI unit for capacitance?

- A. Henry
- B. Volt
- C. Coulomb
- D. Farad

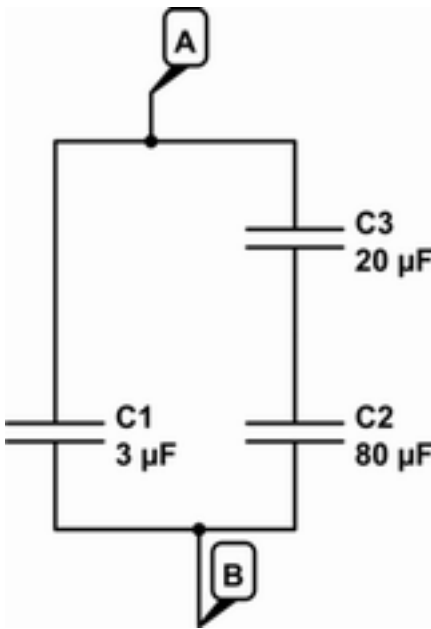9. What is the total capacitance between points A and B?



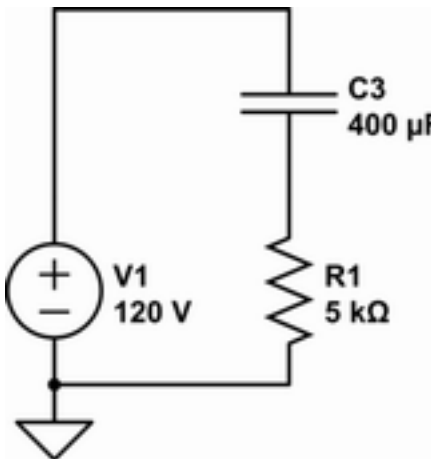10. Find the time constant of the circuit.



11. Which of the following best describes a diode?

- A. a device used to amplify and switch electronic signals and electrical power
- B. an electrical component used to store energy in an electric field
- C. an electrical component with an asymmetric transfer characteristic
- D. a device used to vary the resistance of a circuit

12. EMF stands for...

13. What is Kirchoff's First Law?