

1. 110 ohms
2. 2 A, 1 A, 3 A
3. B
4. 3.3 kohms
5. Fuse - Used to prevent excessive current in a circuit
6. 6V, 1V, 4.5V, 1.5V
7. C
8. D
9. 19 μF
10. 2s
11. C
12. electromotive force
13. Total current entering junction must equal total current exiting junction

Total Points: 19