

December 7th NBMS Invitational Test

1. Please draw the symbols for the following devices (3 points):

Cell	Battery	Voltmeter	Variable Resistor
Bulb	Inductor	Switch	AC Power Source

2. Please define each of the following terms (4 points):

- Electrical Circuit: _____

- Current: _____

 - Direct Current: _____


 - Alternating Current: _____

- Voltage: _____

- Resistance: _____

3. A circuit has two 1.5V AAA batteries placed in series with a 150 kΩ resistor. What is the current that will flow through the circuit? _____ (1-point)

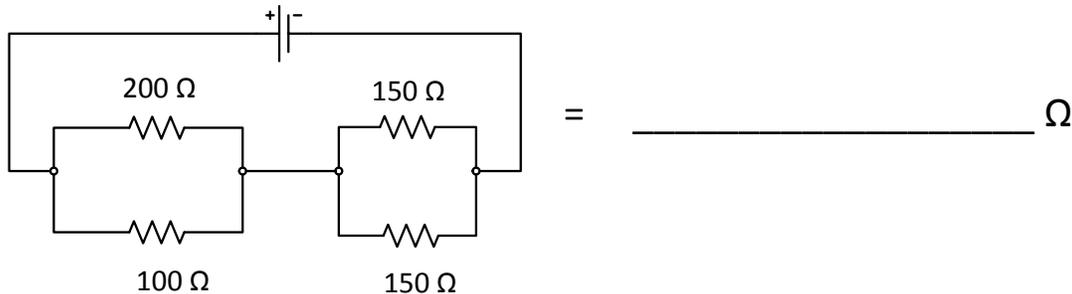4. What is the equivalent resistance of the circuit below (1-point)?




5. In the circuit above, a current of 900mA is measured by adding an Ammeter into the circuit. What is the potential difference generated by the battery? (1-point)

Answer: _____

6. Describe the difference between a **primary battery** and a **secondary battery** (1-point):

Answer: _____

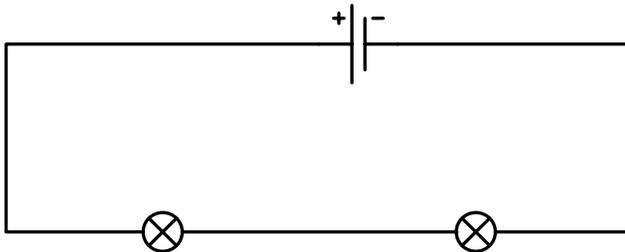
7. Draw the direction of current flow in the following circuit (1-point):



8. If the direction of current flow is reversed, how will the brightness of the bulbs change?

Answer: _____
_____ (1 point)

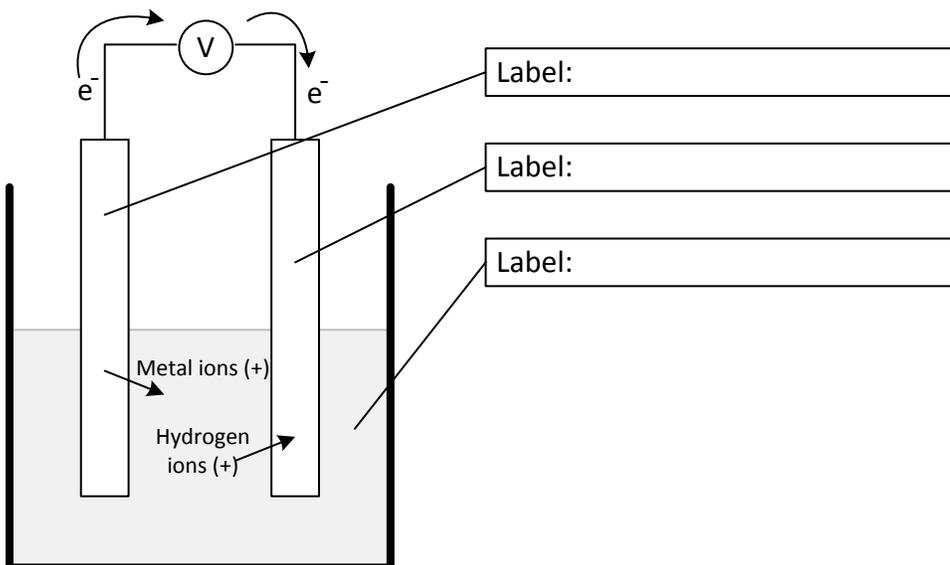9. In the following kitchen-built battery (e.g. lemon battery), please add the missing labels (2 points):




10. A bird decides to land on some high voltage (25kV) power lines. Explain why the bird is not electrocuted (1 point): _____

11. You have created an electromagnet by wrapping some copper wire around a large metal nail. You pass in the current through the copper wire and the electromagnet attracts the North pole of a nearby compass. What happens to the compass if you change the direction of current flowing through the wire (1-point)?

Answer: _____

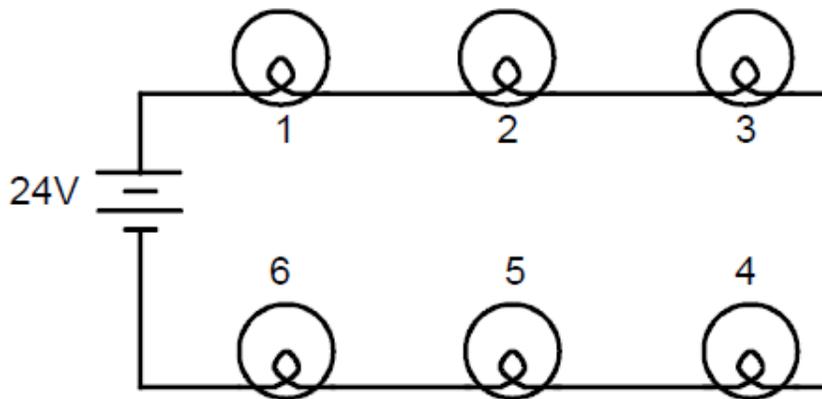12. The short string of Christmas lights below is made up of three different types of bulbs. If bulbs 1 and 4 each have X resistance, bulbs 2 and 5 each have $2X$ resistance, and bulbs 3 and 6 each have $3X$ resistance, what is the voltage drop across each bulb (3-points)?



$V_1 =$ _____ $V_4 =$ _____
 $V_2 =$ _____ $V_5 =$ _____
 $V_3 =$ _____ $V_6 =$ _____