

Names :

Team Name:

Team number:

Captains Test:

Circuit Lab

2018

Answer Sheet

Part 1:

1. _____
2. _____
3. _____
4. _____
5. _____
6. _____
7. _____
8. _____
9. _____
10. _____
11. _____
12. _____
13. _____
14. _____
15. _____
16. _____
17. _____
18. _____
19. _____
20. _____

Part 2

21.

- 1.
- 2.
- 3.
- 4.

22.

23.

24.

25.

26.

- a.
- b.

27.

28.

v1=
v2=

29. V3=


30.

31.

Minimum=

Maximum=

32.

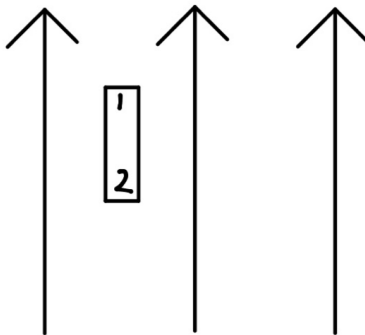

33.

34.

35.

C1

C2

C3

35B.

36.

37.

38.

39.

A

B

C

D

Part B

A

B

C

D

40.

41.